

EE230: Analog Circuits Lab

Lab - 6

Abhineet Agarwal, 22B1219

February 14, 2024

1 Measurement of offset voltage and bias currents


1.1 Measurement of V_{os}

1.1.1 Aim of the experiment

The aim of this experiment was to measure the input offset voltage V_{os} of the given OpAmp IC (LM741 IC).

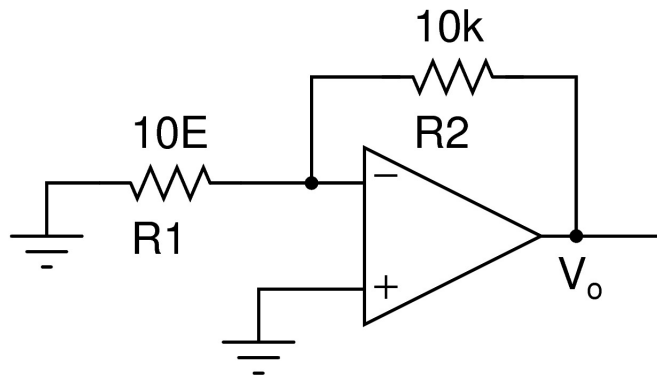1.1.2 Design

The circuit to calculate the input offset voltage is shown in the figure below.




$$R_1 = 10\Omega$$

$$R_2 = 10k\Omega$$

Supply voltages of the Op-Amp = $\pm 15V$

1.1.3 Experimental results

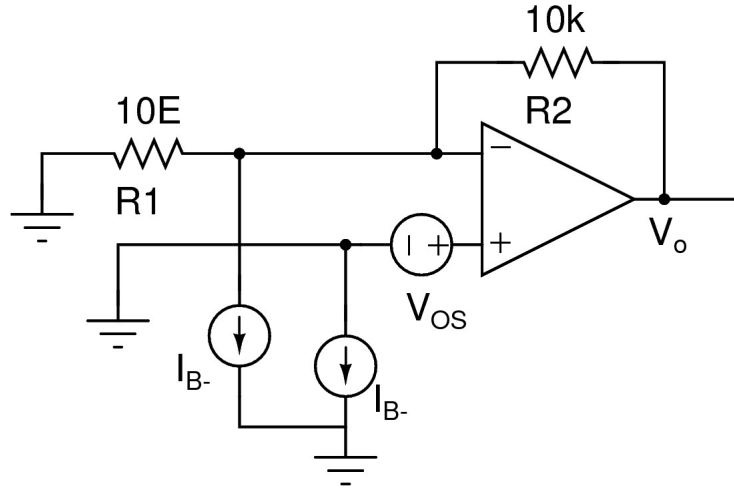- (i) The equivalent circuit, considering the OpAmp non-idealities is shown below:



the output of this circuit is given by:

$$V_o = V_{OS}\left(1 + \frac{R_2}{R_1}\right) + R_2 I_B^-$$

- (ii) For a dominating value of V_{OS} with negligible I_B^- , we can write the above equation as

$$V_{OS} = \frac{V_o}{\left(1 + \frac{R_2}{R_1}\right)} \approx \frac{V_o}{R_2/R_1}$$

- (iii) The values of the resistors used are tabulated below:

	R_1	R_2
theoretical	10Ω	$10k\Omega$
measured	10.2Ω	$9.80k\Omega$

- (iv) Measured output of the circuit $V_o = 1.66V$
 Thus, using the above formula, offset voltage V_{OS}

$$V_{OS} = 1.66mV$$

thus, the measured and the typical datasheet values of the offset voltage are tabulated below:

	V_{OS}
datasheet	$1 - 6mV$
measured	$1.66mV$

1.1.4 Conclusion and Inference

Thus, we measured successfully the offset voltage of the given OpAmp LM741 IC.

1.1.5 Experiment completion status

All parts of this experiment were successfully completed in the lab.

1.2 Measurement of bias current I_B^-

1.2.1 Aim of the experiment


The aim of this experiment was to measure the input bias current in the inverting input I_B^- of the given OpAmp IC (LM741 IC).

1.2.2 Design

The circuit to calculate the input bias current I_B^- is shown in the figure below.


$$R = 10M\Omega$$

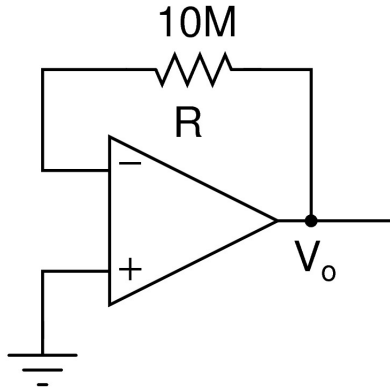Supply voltages of the Op-Amp = $\pm 15V$



1.2.3 Experimental results

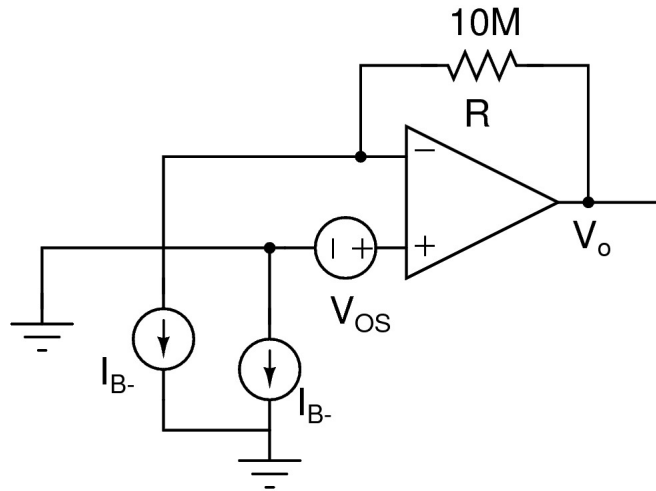- (i) The equivalent circuit, considering the OpAmp non-idealities is shown below:



the output of this circuit is given by:

$$V_o = V_{OS} + I_B^- R$$

- (ii) As the V_{OS} term is very small compared to the value of $I_B^- R$, where $R = 10\text{M}\Omega$, therefore we get

$$I_B^- = \frac{V_o}{R}$$

(iii) The values of the resistor used tabulated below:

	R
theoretical	$10\text{M}\Omega$
measured	$10.1\text{M}\Omega$

(iv) Measured output of the circuit $V_o = 2.34\text{V}$
Thus, using the above formula, offset voltage I_B^-

$$I_B^- = 234\text{nA}$$

thus, the measured and the typical datasheet values of the input bias current are tabulated below:

	I_B^-
datasheet	$80 - 500 \text{ nA}$
measured	234 nA

1.2.4 Conclusion and Inference

Thus, we measured successfully the input bias current in the inverting terminal of the given OpAmp LM741 IC.

1.2.5 Experiment completion status

All parts of this experiment were successfully completed in the lab.

1.3 Measurement of bias current I_B^+

1.3.1 Aim of the experiment


The aim of this experiment was to measure the input bias current in the non-inverting input I_B^+ of the given OpAmp IC (LM741 IC).

1.3.2 Design

The circuit to calculate the input bias current I_B^+ is shown in the figure below.


$$R = 10\text{M}\Omega$$

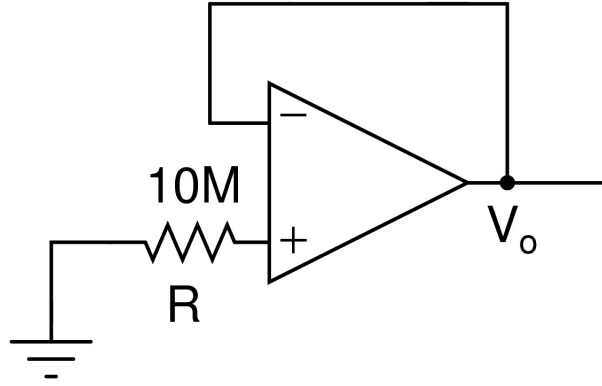Supply voltages of the Op-Amp = $\pm 15\text{V}$



1.3.3 Experimental results

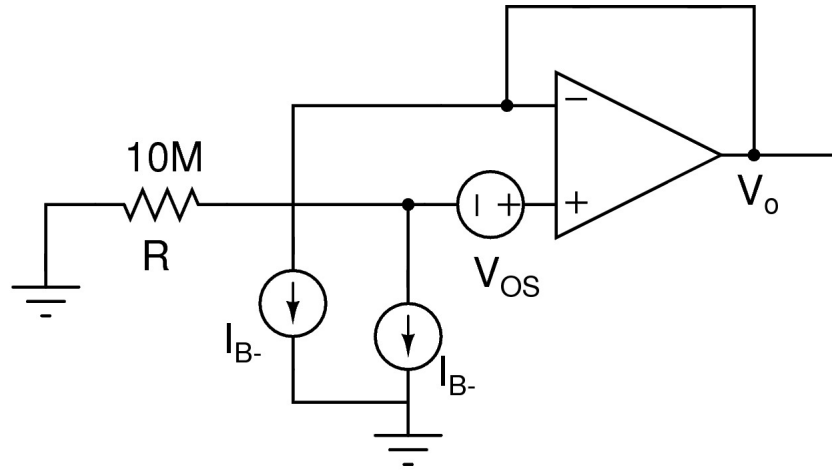- (i) The equivalent circuit, considering the OpAmp non-idealities is shown below:



the output of this circuit is given by:

$$V_o = V_{OS} + I_B^+ R$$

- (ii) As the V_{OS} term is very small compared to the value of $I_B^+ R$, where $R = 10\text{M}\Omega$, therefore we get

$$I_B^+ = \frac{|V_o|}{R}$$

(iii) The values of the resistor used tabulated below:

	R
theoretical	$10\text{M}\Omega$
measured	$10.1\text{M}\Omega$

Measured output of the circuit $V_o = 0.99V$

Thus, using the above formula, offset voltage I_B^+

$$I_B^+ = 99\text{nA}$$

Thus, the measured and the typical datasheet values of the input bias current are tabulated below:

	I_B^+
datasheet	$20 - 200 \text{ nA}$
measured	99 nA

1.3.4 Conclusion and Inference

Thus, we measured successfully the input bias current in the non-inverting terminal of the given OpAmp LM741 IC.


1.3.5 Experiment completion status

All parts of this experiment were successfully completed in the lab.

2 Measurement of Open-loop gain

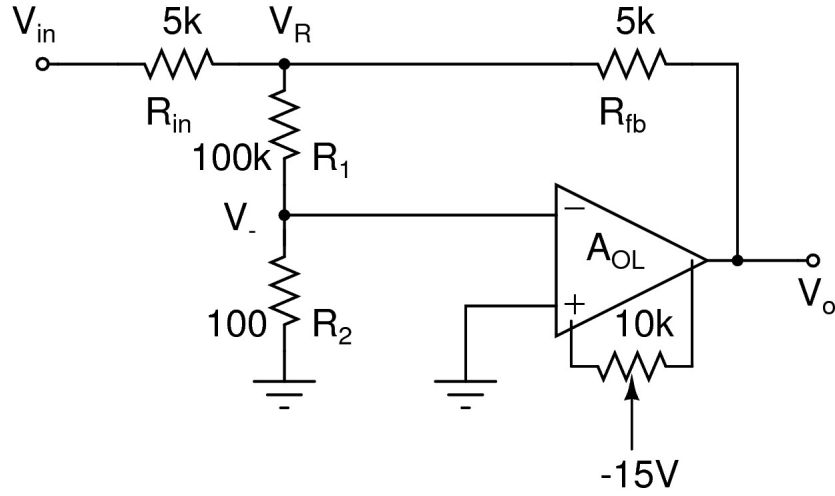2.1 Aim of the experiment

The aim of this experiment was to measure the open-loop gain of the given OpAmp LM741 IC, and to analyse its frequency response.



2.2 Design

The OpAmp configuration used to measure the open-loop gain is shown below.

$$R_{in} = R_{fb} = 5k\Omega$$

$$R_1 = 100k\Omega$$

$$R_2 = 100\Omega$$

10kΩ pot. was used for offset voltage nullification

Supply voltages of the Op-Amp = $\pm 15V$

2.3 Experimental results

(i) The values of the resistors used in the given circuit are tabulated below:

	theoretical	measured
R_{in}	$5k\Omega$	$5k\Omega$
R_{fb}	$5k\Omega$	$5k\Omega$
R_1	$100k\Omega$	$99.7k\Omega$
R_2	100Ω	99.8Ω

(ii) Connecting the 10k pot. across the offset null pins, and connecting the variable leg of the pot. to V_{EE} , we adjust the pot. appropriately so that output $V_o = 0V$ for $V_{in} = 0V$.

The value of V_o after nullifying the offset = $0.01V$

- (iii) For $V_{in} = 1V$, the observed $V_o = -1.010V$.
 As the measured value is almost same as the expected output $V_o = -1V$, thus this verifies that the offset has been nullified and that the circuit is connected properly.
- (iv) For $V_{in} = 15V_{pp}$, the measured peak-to-peak V_R and V_o , and the calculated gain A_{OL} is given by:

$$|A_{OL}| = \frac{|V_o|}{|V_R|} \frac{R_1 + R_2}{R_2}$$

Tabulated measurements of the same are given below:

f	$V_{o(pp)}$	$V_{R(pp)}$	A_{OL}
10 kHz	880 mV	7.28 V	120.9
1 kHz	6.48 V	6.72 V	964.2
500 Hz	10.4 V	5.52 V	1884.1
100 Hz	14.8 V	1.64 V	9024.3
20 Hz	15.0 V	336 mV	44642.8
10 Hz	15.2 V	180 mV	84444.4
9 Hz	15.2 V	172 mV	88372.09
8 Hz	15.2 V	140 mV	108571.4
7 Hz	15.2 V	124 mV	122580.6
6 Hz	15.2 V	164 mV	92682.9
5 Hz	15.2 V	88 mV	172727
4 Hz	15.2 V	72 mV	211111
3 Hz	15.2 V	60 mV	253333
2 Hz	15.2 V	44 mV	345454
1 Hz	15.2 V	36 mV	506666

Table. Open-Loop Gain

(v) Now,

From the tabulated values, the maximum gain $A_{OL(max)} = 506666$

Now,

$\frac{1}{\sqrt{2}}$ (approximately 70.7%) of this maximum gain $A_{OL(max)} \approx 358266.96$

This value of gain occurs around 2 Hz

Thus, the 3-dB frequency (Bandwidth of the OpAmp) ≈ 2 Hz

(vi) Roll-off slope = gain at 10kHz - gain at 1kHz (in dB)

Hence,


Roll-off slope = -29.3 dB/decade

Observed from the table, the given system has 1 pole, with a pole frequency ≈ 4 Hz.

(vii) Thus, the measured and the typical datasheet values of the open-loop gain A_{OL} and 3-db frequency are tabulated below:

	A_{OL}	3-db freq.
datasheet	2×10^5	7.5Hz
measured	$\approx 5 \times 10^5$	≈ 2 Hz

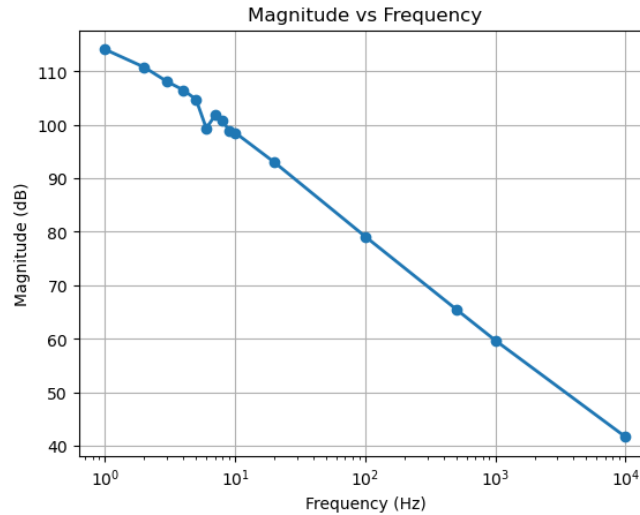(viii) Magnitude frequency response of A_{OL} (Bode Plot) is given below:



2.4 Conclusion and Inference

Thus, we measured the open-loop gain of the given OpAmp IC successfully and analysed it's frequency response.

2.5 Experiment completion status

All parts of this experiment were successfully completed in the lab.

Parameters of the LM741 IC

The comparison between the measured and typical datasheet values of the parameters of the LM741 IC is tabulated below:

	datasheet	measured
V_{OS}	1-6 mV	1.66 mV
I_B^-	80-500 nA	234 nA
I_B^+	20-200 nA	99 nA
A_{OL}	2×10^5	$\approx 5 \times 10^5$
f_{3dB}	7.5 Hz	≈ 2 Hz