

# EE230: Analog Circuits Lab

## Lab No.5

Abhineet Agarwal, 22B1219

February 7, 2024

## 1 Hardware Implementation of an Analog Square-root Circuit

### 1.1 Aim of the experiment

To understand the Log and Antilog amplifier to make a square root amplifier.

### 1.2 Design

The circuit is interconnected block by block, as depicted in the figure. The voltages  $V_{b1}$  and  $V_{b2}$  are generated using potentiometers connected between  $V_{CC} = +15V$  and ground.

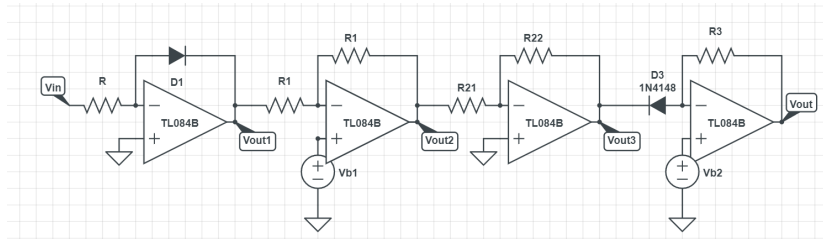


Figure 1: Analog square-root circuit

### 1.2.1 Section 1

A connection is established between the ground and  $V_{CC}$  through a potentiometer, with its central pin linked to the non-inverting terminal of the LM-741 Op-Amp IC. The inverting terminal and output of the 741-IC are interconnected and directed to  $R$  in Block 1.

### 1.2.2 Section 2

The inverting terminal of the Op-Amp is linked to  $R$ , while the non-inverting terminal is grounded. The positive side of diode  $D1$  is connected to the inverting terminal of the Op-Amp, and the negative side is connected to the Op-Amp's output. The output of the Op-Amp is then connected to  $R_1$ .

$$R = 2.23 \text{ k}\Omega \quad (1)$$

### 1.2.3 Section 3

The inverting terminal of the Op-Amp is connected to  $R_1$ , and the non-inverting terminal is set to  $V_{b1}$ . The output of the Op-Amp is connected to  $R_{21}$ .

$$R_1 = 2 \text{ k}\Omega \quad (2)$$

$$R_{21} = 3 \text{ k}\Omega \quad (3)$$

Set  $V_{in}$  as 1V and change  $V_{b1}$  till  $V_{out2} = 0V$ .

### 1.2.4 Section 4

The inverting terminal of the Op-Amp is connected to  $R_{21}$ , and the non-inverting terminal is grounded, as shown in Fig.  $R_{22}$  is connected between the inverting terminal and the output of the Op-Amp. The output is also linked to the cathode of diode  $D2$ .

$$\begin{aligned} R_{22} &= R_{21}\beta \\ &= R_{21}b_2 \frac{n_2}{n_1} \end{aligned} \quad (4)$$

For square root amplifier  $b_2 = \frac{1}{2}$  and  $n_1 \approx n_2$

$$\begin{aligned} R_{22} &= \frac{R_{21}}{2} \\ &= 2.013k \text{ } k\Omega \end{aligned} \tag{5}$$

$R_{22}$  can varied to get different powers of  $V_{in}$  at the output.

### 1.2.5 Section 5

The Op-Amp's inverting terminal is linked to the anode of diode  $D2$ , while the non-inverting terminal is set to  $V_{b2}$ .  $R_3$  is positioned between the inverting terminal and the Op-Amp's output. The output of the square-root amplifier is obtained across resistor  $R_3$ . The resistor's resistance is adjusted to ensure diode  $D2$  operates in the linear region.  $V_{b2}$  is varied until  $V_{out} = 1V$  for  $V_{in} = 1V$ .

$$R_3 = 0.827 \text{ } k\Omega \tag{6}$$

## 1.3 Simulation Results

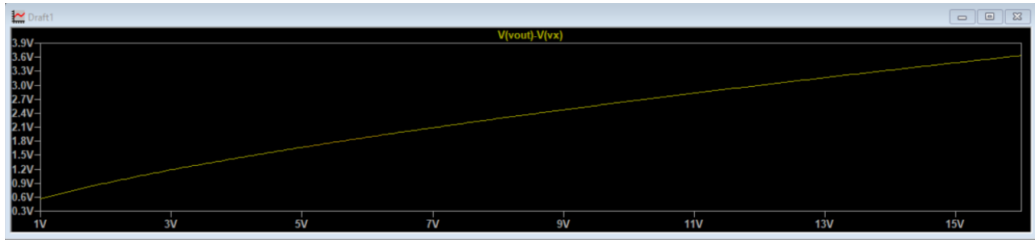


Figure 2:  $V_{out}$

## 1.4 Experimental Results

Q1. Block 0 is used to implement the potentiometer which is used to give a large range of DC voltage from 0 to  $+V_{CC} = 15V$ .

Q2. If  $V_{in}$  is directly connected to  $V_{in1}$  then current will flow from resistor  $R$  which changes the input voltage, changing the output - input relation.

Q3.

$$\text{Input Current} = \frac{V_{in}}{R} \quad (7)$$

$$\text{Input Voltage} = V_{in} \quad (8)$$

$$\begin{aligned} \text{Input Impedance} &= \frac{V_{in}}{I_{in}} \\ &= R \end{aligned} \quad (9)$$

Q6.

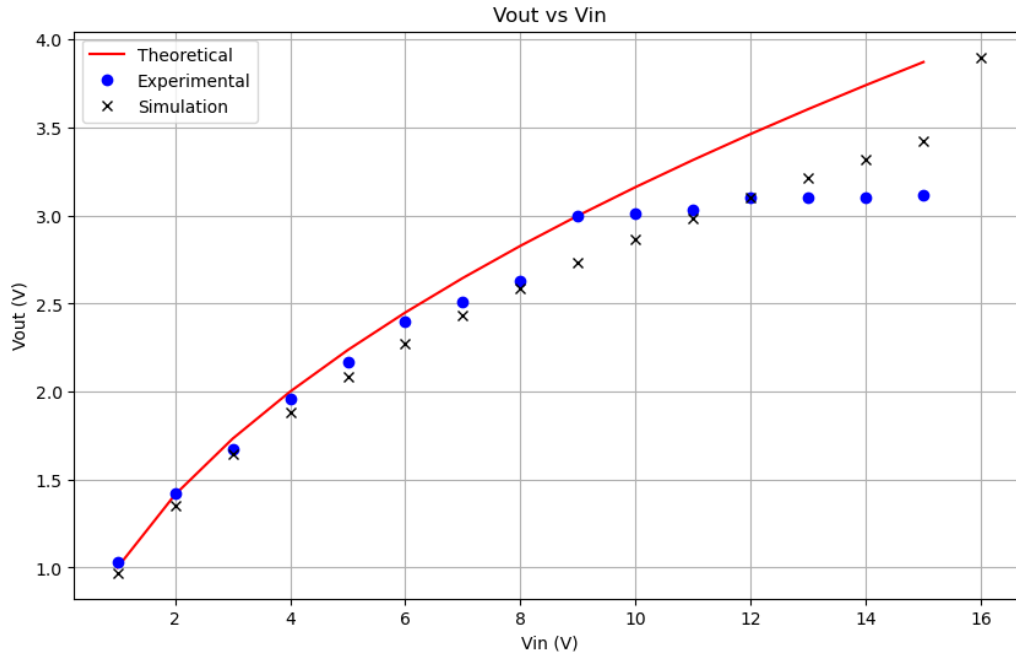


Figure 3: Simulated, Observed and Theoretical  $V_{outs}$  plotted against  $V_{in}$

$$V_{b1} = -0.28V \quad (10)$$

$$V_{b2} = 0.6V \quad (11)$$

Q7.  $V_{R_3} = V_{out4} - V_{out3}$  but since  $V_x = V_{b2}$  due to virtual ground between inverting and non-inverting terminal of the Op-Amp.

$$V_{R_3} = I_{S_2} R_3 e^{V_{b2}/n_2 V_T} (V_{in})^{n_1 \beta / n_2} \quad (12)$$

$V_{b2}$  is important to ensure correct biasing of diode.  $R_3$  is for fine adjustment as  $V_{R_3} \propto R_3 \propto \sqrt{V_{in}}$ . Thus the potentiometer at the non-inverting terminal acts as a coarse adjustment, whereas the feedback resistor( $R_3$ ) acts as a fine adjustment.

Q8.

Table 1: Observed Values fro  $V_{out}$

| $V_{in}$ | $V_{out}$ |
|----------|-----------|
| 1 V      | 1.03 V    |
| 2 V      | 1.42 V    |
| 3 V      | 1.67 V    |
| 4 V      | 1.96 V    |
| 5 V      | 2.17 V    |
| 6 V      | 2.40 V    |
| 7 V      | 2.51 V    |
| 8 V      | 2.63 V    |
| 9 V      | 3 V       |
| 10 V     | 3.01 V    |
| 11 V     | 3.03 V    |
| 12 V     | 3.10 V    |
| 13 V     | 3.10 V    |
| 14 V     | 3.10 V    |
| 15 V     | 3.12 V    |

Q9. Refer figure 8

Q10. Refer figure 9

Q11.

$$V_{out} = (V_{in})^{\frac{1}{2}} \quad (13)$$

$$\ln(V_{out}) = \frac{\ln(V_{in})}{2} \quad (14)$$

Therefore expected slope of  $\ln(V_{out})$  vs  $\ln(V_{in})$  graph =  $\frac{1}{2}$

Q12. If the polarity of the diode D2 is reversed then  $V_{out}$  would not be proportional to positive power of  $V_{in}$ . The graph would be similar to  $\frac{1}{\sqrt{V_{in}}}$

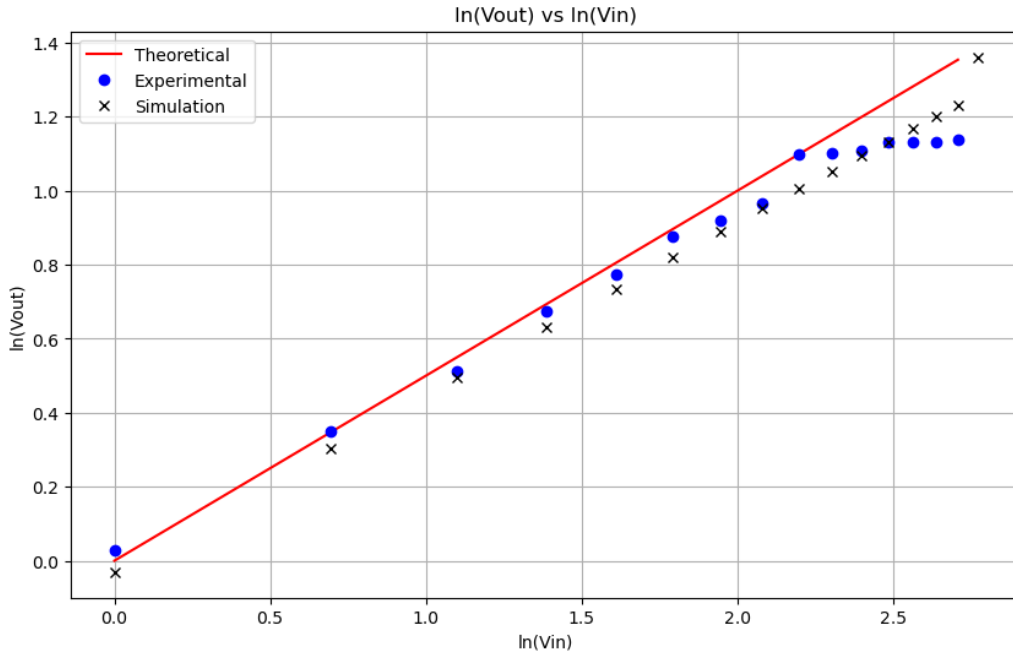


Figure 4: Simulated, Observed and Theoretical  $\ln(V_{out})$ s plotted vs  $\ln(V_{in})$

## 1.5 Conclusion and Inference

- Potentiometers can be used to implement variable voltage source and variable resistors.
- The current conducted through a diode depends on voltage across it exponentially when it is not in saturation.
- OpAmps can be used as a Logarithmic amplifier with a non-ideal diode.

- OpAmps can be used as an Anti-logarithmic amplifier with a non-ideal diode..

## **1.6 Experiment completion status**

Completed the experiment in its entirety in lab. Competed all sections and found answers to all the questions in the lab sheet.