

# EE230: Analog Circuits Lab

## Lab No. 10-11

Abhineet Agarwal, 22b1219

April 3, 2024

## 1 Differential Amplifier with Resistive Load

### 1.1 Aim of the experiment

Simulating and experimenting with a differential amplifier circuit with a resistive load, amplifying the small signal AC component of the input Voltage.


### 1.2 Design

For the circuit, the differential gain,  $A_v$  is given by:

$$A_v = R_2 * \sqrt{I_{tail} K_{n1}} \quad (1)$$

and the output common mode voltage is:
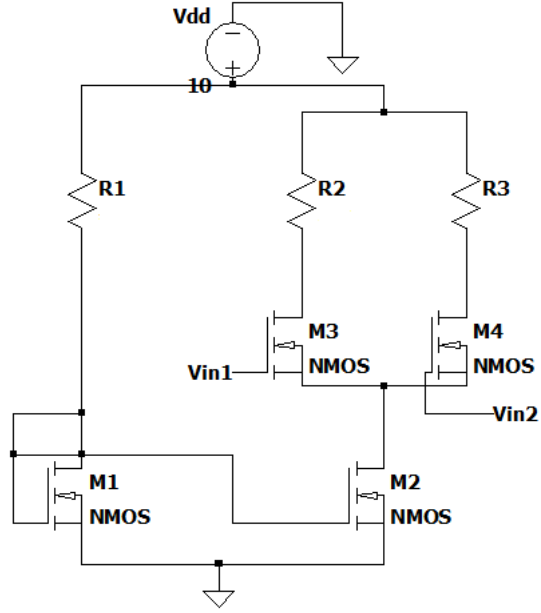
$$V_{outcm} = V_{DD} - \frac{I_{tail} R_2}{2} \quad (2)$$



### 1.3 Simulation

For the specifications:

Gain > 12dB

,  $V_{incmin} = 3.5V$

and  $5V < V_{outcmin} < 7V$

and keeping  $K_n = 0.53mA/V^2$ ,  $K_p = 0.16mA/V^2$ ,  $V_{thn} = 0.45V$ ,  $V_{thp} = -0.5V$ .

Choosing the following values:

$$A_v = 5$$

$$R_2 = R_3 = 7.47k\Omega$$

$$V_{outCM} = 6.84V$$

$$I_{tail} = 0.846mA$$

$$R_1 = 9.17k\Omega$$

$V_{GS1} = V_{DS1} = V_{GS2}$	2.23V
$V_{DS2}$	2.8V
$V_{out1}$	6.83V
$V_{out2}$	6.83V
$I_{ref}$	0.846mA

## 1.4 Simulation Results

### 1.4.1 Large signal(DC) response

#### 1.4.2 Vin1 sweep

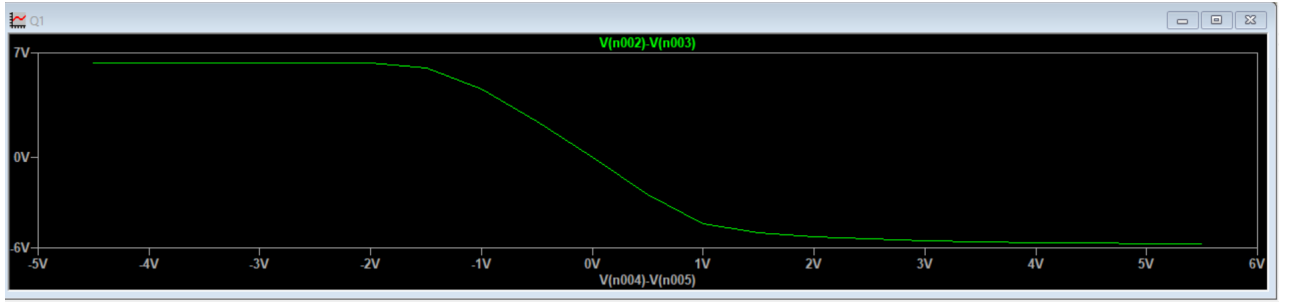


Figure 1: ( $V_{out1} - V_{out2}$ ) vs ( $V_{in1} - V_{in2}$ )

### 1.4.3 Small signal(AC) response

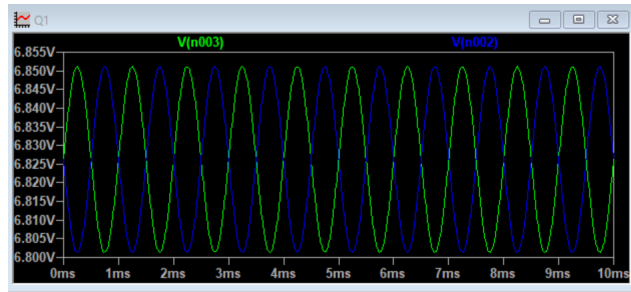


Figure 2:  $V_{out1}$  and  $V_{out2}$

So the small signal gain comes out to be:

$$A_v = 5 \quad (3)$$

## 1.5 Experiment Results

### 1.5.1 Large signal analysis

$$V_{in1} = V_{in2} = 4.5V$$

The following values were observed:  $V_{out1} = 6.36V$

$$V_{out2} = 6.75V$$

All MOSFETS were observed to be in saturation.

### 1.5.2 Small Signal Analysis

$$V_{in1} = 20 \text{ mVpp, 1kHz sinusoid with 4.5 DC offset}$$

$$V_{in2} = 20 \text{ mVpp, 1kHz sinusoid with 4.5 DC offset, out of phase with } V_{in1}$$

The following values were observed:

$$V_{out1} = 112 \text{ mVpp, 1kHz sinusoid}$$

$$V_{out2} = 112 \text{ mVpp, 1kHz sinusoid out of phase with } V_{out1}$$

We observed a 180 degree phase shift as well. So the small signal gain comes out to be:

$$A_v = \frac{112}{20} = 5.6 \quad (4)$$

## 1.6 Conclusion and Inference

This experiment demonstrated the method to bias a MOSFET in the correct region (saturation), and also demonstrated the construction of a differential amplifier with a resistive load.

## 1.7 Experiment completion status

Completed.



where

$$r_o = \frac{1}{\lambda I_D} \quad (6)$$

and the output DC mode voltage is:

$$V_{outDC} = V_{DD} - \sqrt{\frac{I_o}{K_n}} - V_{th} \quad (7)$$

## 2.3 Simulation

For the specifications:

$$V_{outDC} = 6V$$

$$V_{DD} = 10V$$

we get

$$5.1V < V_{incm} < 6.45V$$

and keeping  $K_n = 0.53mA/V^2$ ,  $K_p = 0.16mA/V^2$ ,  $V_{thn} = 0.45V$ ,  $V_{thp} = -0.5V$ .

$$I_o = 1.96mA$$

$$R_D = 3.48k\Omega$$



$$V_{D05} = 3.63V$$

$$V_{incm} = 5.7V$$

## 2.4 Simulation Results

### 2.4.1 Large signal(DC) response

$V_{in1} = V_{in2}$	5.7V
$V_{DS5}$	3.15V
$V_{GS0}$	3.15V
$V_{DS0}$	3.337V
$V_{out}$	6.03V
$V_{g3}$	6.03V

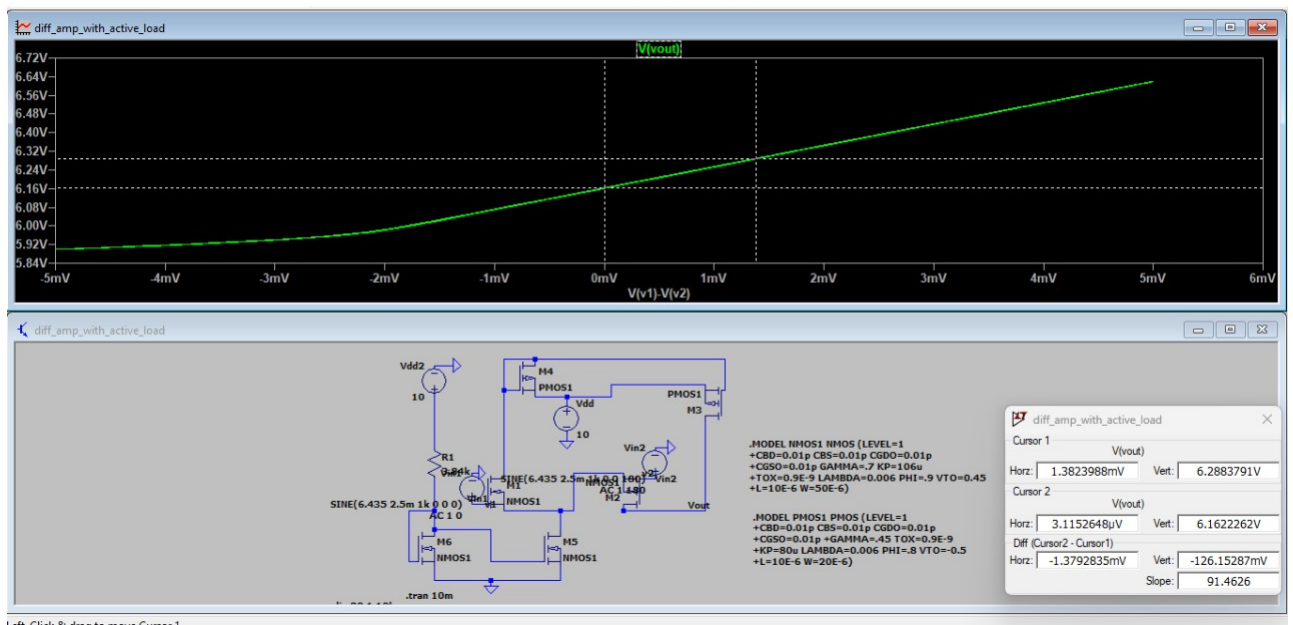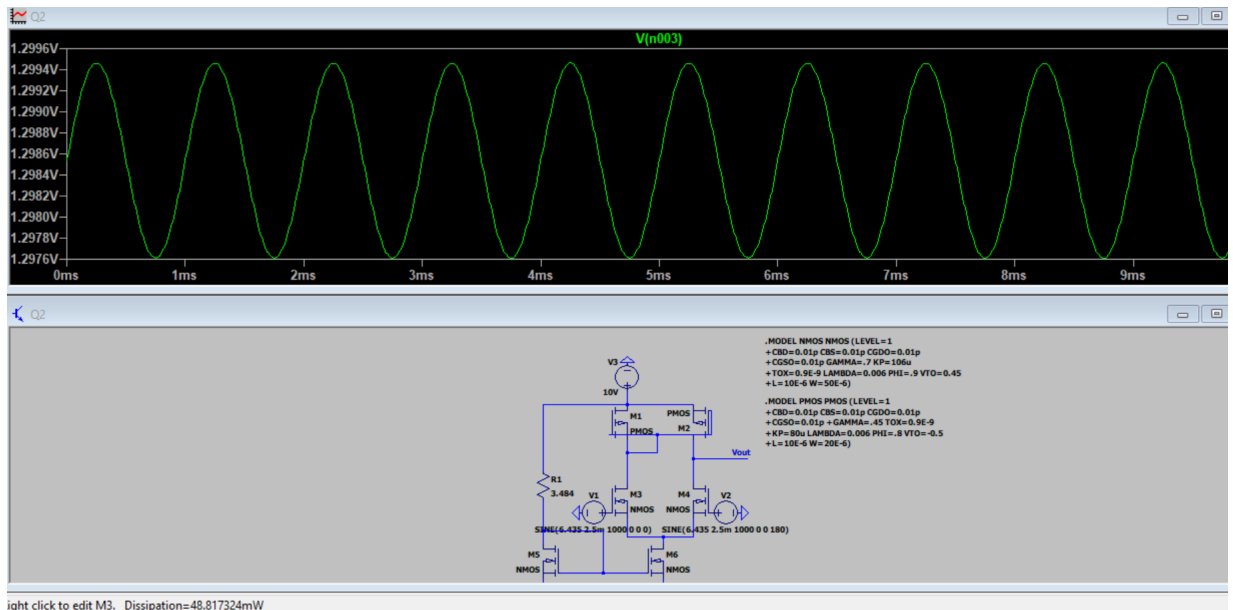



### 2.4.2 Small signal(AC) response

So the small signal gain comes out to be:

$$A_v = 86.80 \quad (8)$$

While the hand calculated value is 86.67, which is pretty close to this value.

### 2.4.3 Common mode gain

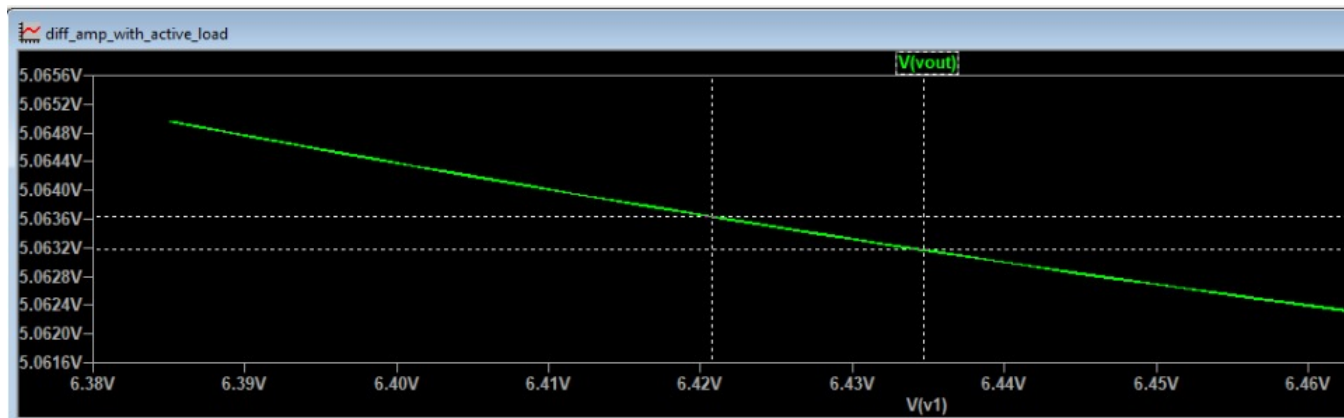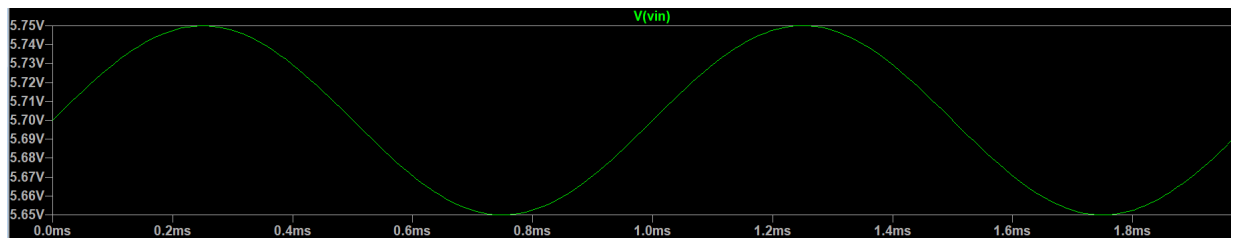

Which gives the common mode gain = 0.01.



## 2.5 Experiment Results

### 2.5.1 Large signal analysis

$$V_{in1} = V_{in2} = V_{inCM} = 5.5V$$

$$V_{out} = 6.4V$$

$$V_{gs} = 2V$$

$$V_{ds} = 4.1V$$

$$I_{ref} = 1.27mA$$

All MOSFETs observed to be in saturation.

### 2.5.2 Small Signal Analysis

$V_{in1}$  = 20 mVpp, 1kHz sinusoid with 5.5V DC offset

$V_{in2}$  = 20 mVpp, 1kHz sinusoid with 5.5V DC offset, out of phase with  $V_{in1}$

The following values were observed:

$V_{out}$  = 3.3Vpp, 1kHz sinusoid, with an offset of 5.9 V. So the small signal gain comes out to be:

$$A_v = \frac{3.3}{0.04} = 85 \quad (9)$$

All MOSFETS were observed to be in saturation.

## 2.6 Conclusion and Inference

This experiment demonstrated the method to bias a MOSFET in the correct region, and also demonstrated how to build a differential amplifier with diode connected load.


## 2.7 Experiment completion status

Completed.




### 3.2.2 Simulation

Vin DC SWEEP

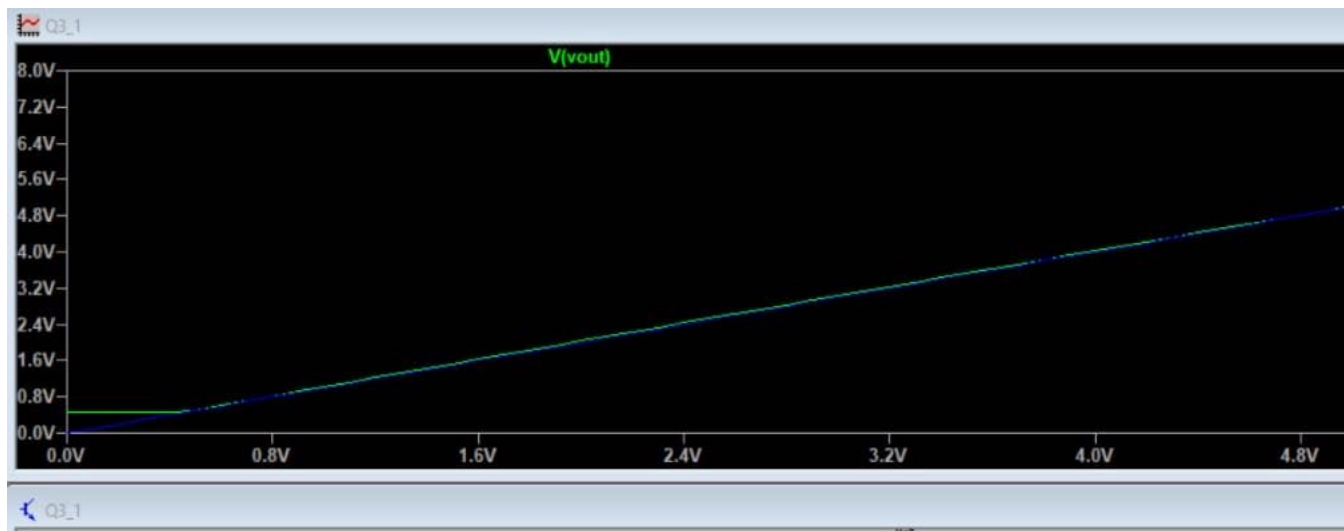

SINUSOIDAL INPUT

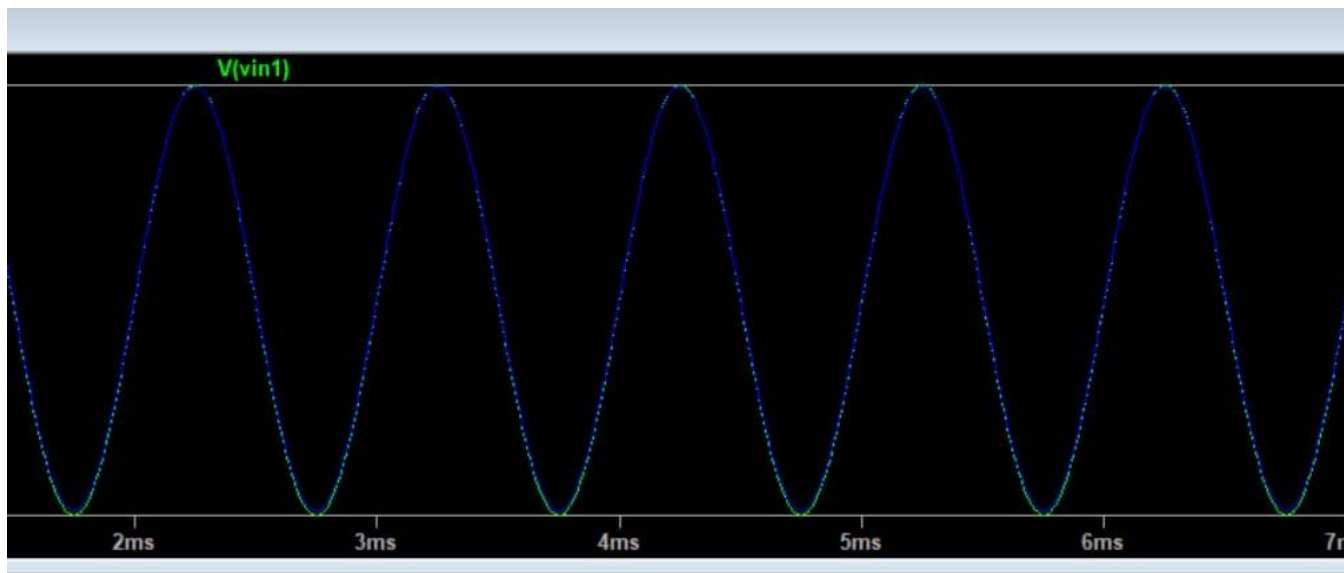

### 3.2.3 Experimental Results


$$R_D = 3.4\text{k}\Omega$$


$V_{in}$  = sinusoid of 1V peak to peak amplitude, 1kHz frequency and an offset of 5.5V

$V_{outAC}$  = sinusoid with 1V peak to peak, from 5.53 to 6.53 V.

## 3.3 Inverting Amplifier

### 3.3.1 Design

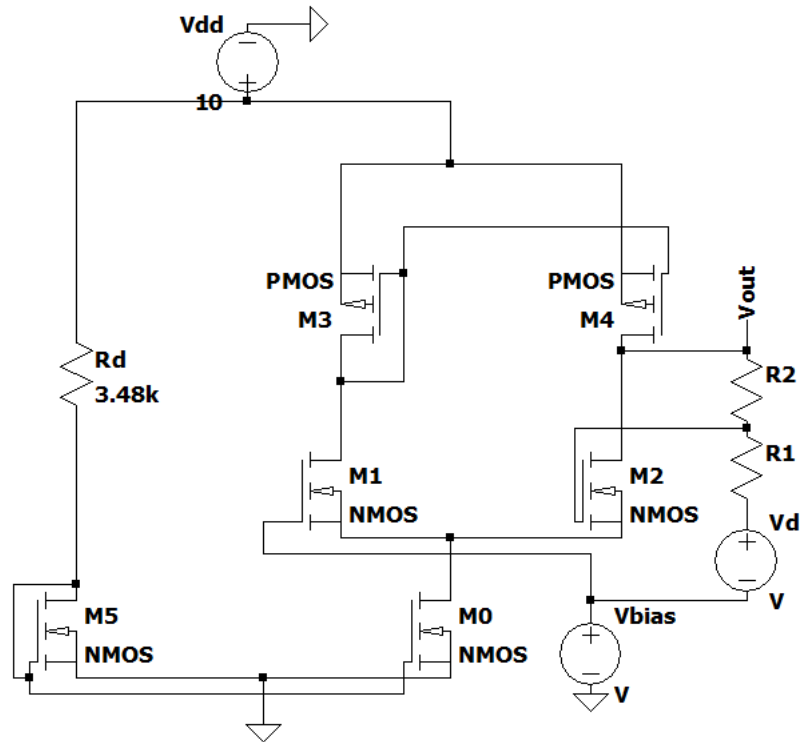

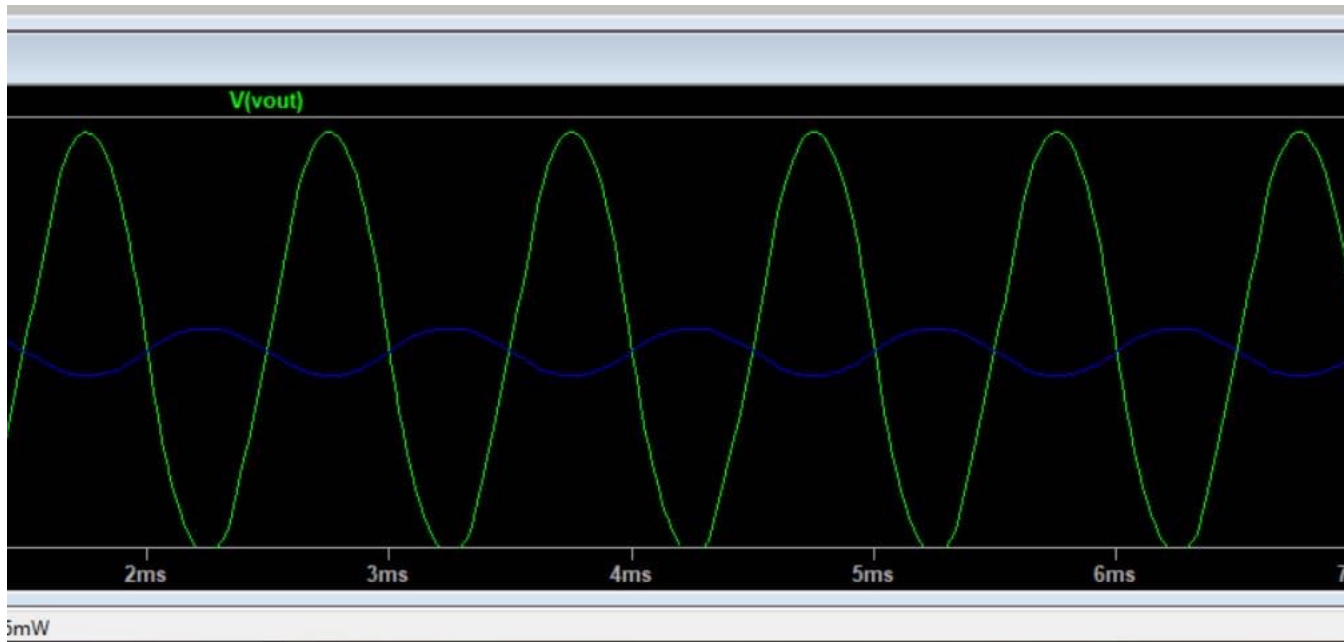

### 3.3.2 Simulation

### 3.3.3 Experimental Results

$$V_{bias} = 5.5V$$

$$R_2 = 10 \text{ M}\Omega$$

$$R_1 = 1 \text{ M}\Omega$$

$$V_d = 50 \text{ mVpp, 1kHz sinusoid}$$

The output observed was a 499.2 mVpp, 1kHz sinusoid


So the gain is  $A_v = -167$  degrees

## 3.4 Differentiator
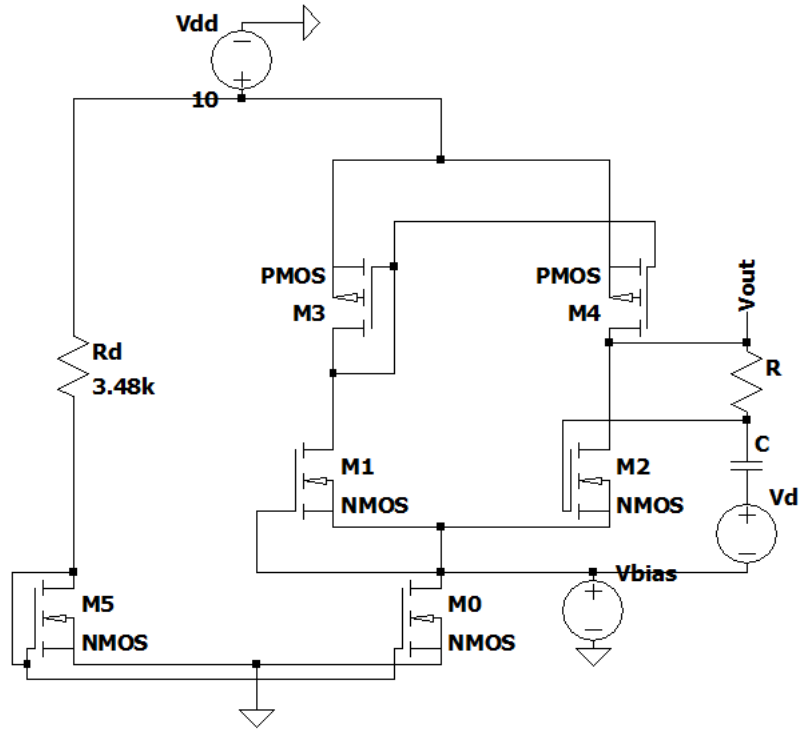
### 3.4.1 Design


for this circuit:

$$V_{outpp} = \frac{f * V_{inpp}}{250} \text{ where } f = \text{frequency (Hz) of the input waveform}$$


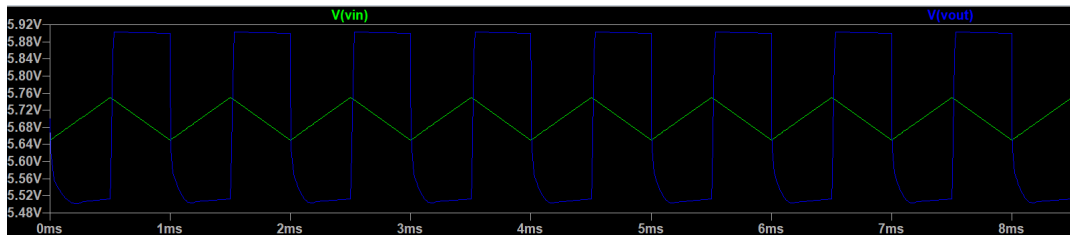
### 3.4.2 Simulation

Keeping  $V_{in}$  as triangular waveform of 100 mVpp, 1 KHz frequency, with  $C = 100\text{pF}$ ,  $R = 10\text{M}\Omega$



### **3.4.3 Experimental Results**

For  $V_{in} = 100\text{mV}_{pp}$ , 1kHz sinusoid,  $V_{out} = 400\text{mV}_{pp}$ , we observed a triangular waveform from 5.97 V to 6.10 V.

## **3.5 Conclusion and Inference**

This experiment demonstrated the method to bias a MOSFET in the correct region, and also demonstrated a unity gain amplifier, an inverting amplifier and a differentiator circuit, using a 5T-OTA circuit.

## **3.6 Experiment completion status**

Completed.